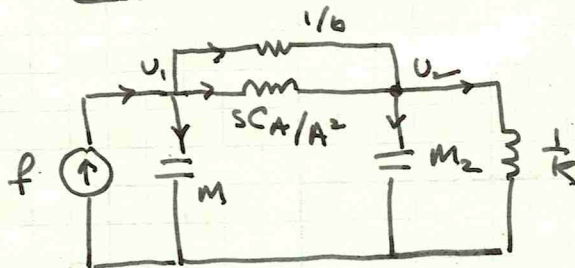


$$C_A = \frac{A^2}{\rho C^2}$$



(b)

$$F = \frac{U_1 - U_2}{\frac{1}{b}} + \frac{M \dot{u}_1}{1} + \frac{U_1 - U_2}{\frac{s C_A}{A^2}} \Rightarrow \dot{F} = b(\dot{u}_1 - \dot{u}_2) + M \dot{u}_1 + (u_1 - u_2) \frac{A^2}{C_A}$$

$$\frac{U_1 - U_2}{\frac{s C_A}{A^2}} + \frac{U_1 - U_2}{\frac{1}{b}} = \frac{U_2}{\frac{1}{M_2 s}} + \frac{U_2}{\frac{s}{k}} \Rightarrow (u_1 - u_2) \frac{A^2}{C_A} + b(u_1 - u_2) = \dot{u}_2 M_2 + u_2 k$$


(c)

$$U_1 \left[\frac{A^2}{C_A} + b s \right] = U_2 \left[s^2 M_2 + b s + k + \frac{A^2}{C_A} \right]$$

$$\frac{U_2}{U_1} = \left[\frac{\frac{A^2}{C_A} + b s}{s^2 M_2 + b s + k + \frac{A^2}{C_A}} \right]$$

2

(a)

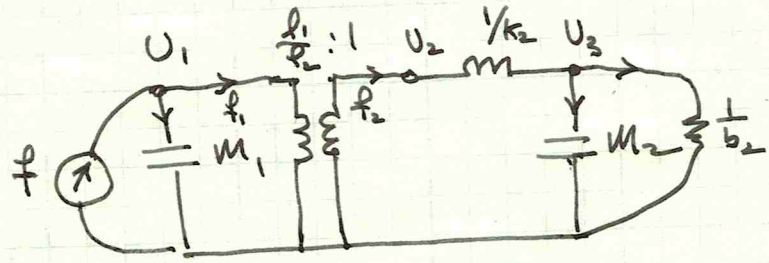

(b) node U_1 :
$$F = \frac{U_1}{\frac{1}{M_1 S}} + F_1$$

transformer:
$$F_1 \frac{l_1}{l_2} = F_2$$

$$U_1 \frac{l_2}{l_1} = U_2$$

$$F_2 = \frac{U_2 - U_3}{\frac{1}{k_2}}$$

unknowns: U_1, U_2, U_3
 F_1, F_2 ✓

node U_3 :
$$F_2 = \frac{U_3}{\frac{1}{M_2 S}} + \frac{U_3}{\frac{1}{b_2}}$$

$$f = M_1 \dot{u}_1 + f_1$$



$$f_1 \frac{l_1}{l_2} = f_2$$

$$u_1 \frac{l_2}{l_1} = u_2$$

$$f_2 = k_2 (u_2 - u_3)$$

$$f_2 = \dot{u}_3 M_2 + \frac{1}{b_2} u_3$$

3.

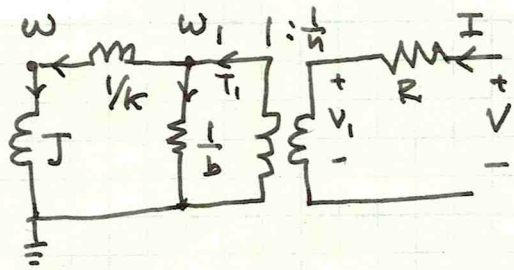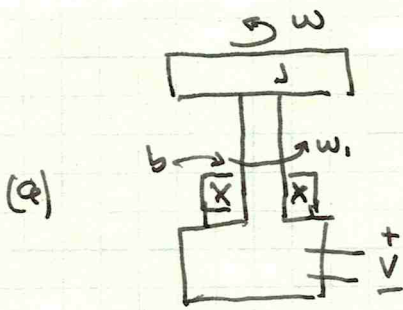

$$I = \frac{V - V_1}{R}$$

$$I \frac{1}{n} = T_1$$

$$V_1 n = w_1$$

$$T_1 = \frac{w_1}{\frac{1}{b}} + \frac{w_1 - w}{\frac{1}{ks}}$$

$$\frac{w_1 - w}{\frac{1}{ks}} = \frac{w}{\frac{1}{Js}}$$

$$i = \frac{V - V_1}{R}$$


$$i \frac{1}{n} = T_1$$

$$V_1 n = w_1$$

$$\dot{T}_1 = b \dot{w}_1 + [w_1 - w] k$$

$$(w_1 - w) k = \dot{w} J$$

(c) $k \rightarrow \infty$

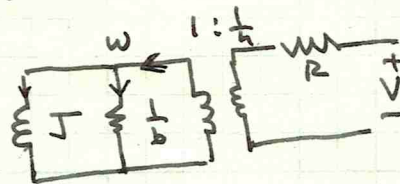

$$\dot{w} J + b w = 0 \Rightarrow J [s \bar{W} - w(0)] + b \bar{W} = 0$$

$$V n = w$$

$$[J s + b] \bar{W} - J w(0) = 0$$

$$\bar{W} = \frac{w(0)}{s + \frac{b}{J}}$$

$$w(t) = w(0) e^{-\frac{b}{J} t} \quad t \geq 0$$

$$\Rightarrow V = \frac{w}{n} = \frac{w(0)}{n} e^{-\frac{b}{J} t}$$